 



DSD_Final

這次我們主要要實做的事 pipeline，而 pipeline 的好處就在於它可以把過程分成好幾個階段，不會像一般的程式，需要等到一個城市跑完之後才可以去跑下一個，以右圖為例；



可以看見，節省了許多時間，所以我這次設計的概念，就是依照老師講義上的圖，把流程分成了 4 個 state，IF、DOF、EXE、WB。

 第一階段，IF_state，就是從 I_memory 中讀取這一個 cycle 所需要的值出來，之後則會把這個 instruction 丟到下一個 state，也就是 DOF_state，這個 state，主要是把 instruction decode 出來，然後把下一個 EXE_state 需要用到的東西，傳下去，而 MUXA 和 MUXB 所選出來的東西，則是會看你的 instruction，是做 R_type 或者 I_type 或是 others。



```

1      Register_File Register_file(
      .clk(clk),
      .rst_n(rst_n),
      .instruction(instruction),
      .AA(DOF_AA),
      .BA(DOF_BA),
      .BUS_D(BUS_D),
      .RW(WB_RW),
      .DA(WB_DA),
      .A_data(A_data),
      .B_data(B_data)
);

1      Decoder instruction_decode(
      .clk(clk),
      .rst_n(rst_n),
      .instruction(instruction),
      .flush(IC_sel),
      .RW(DOF_RW),
      .MD (DOF_MD),
      .BS (DOF_BS),
      .PS (DOF_PS),
      .MW (DOF_MW),
      .FS (DOF_FS),
      .MB (MB),
      .MA (MA),
      .CS (CS),
      .DA (DOF_DA),
      .AA (DOF_AA),
      .BA (DOF_BA)
);

```

```

MUX_A Mux_A(
.clk(clk),
.rst_n(rst_n),
.EX_Hazard_A(EX_Hazard_A),
.WB_Hazard_A(WB_Hazard_A),
.Forward(Forward),
.BUS_D(BUS_D),
.pc_1(pc_1),
.A_data(A_data),
.MA(MA),
.Bus_A(Bus_A),
.EX_MD(EX_MD)

) ;

```


```

MUX_B Mux_B(
.constant(constant),
.B_Data(B_data),
.MB(MB),
.Bus_B(Bus_B),
.EX_Hazard_B(EX_Hazard_B),
.WB_Hazard_B(WB_Hazard_B),
.Forward(Forward),
.BUS_D(BUS_D)

) ;

```

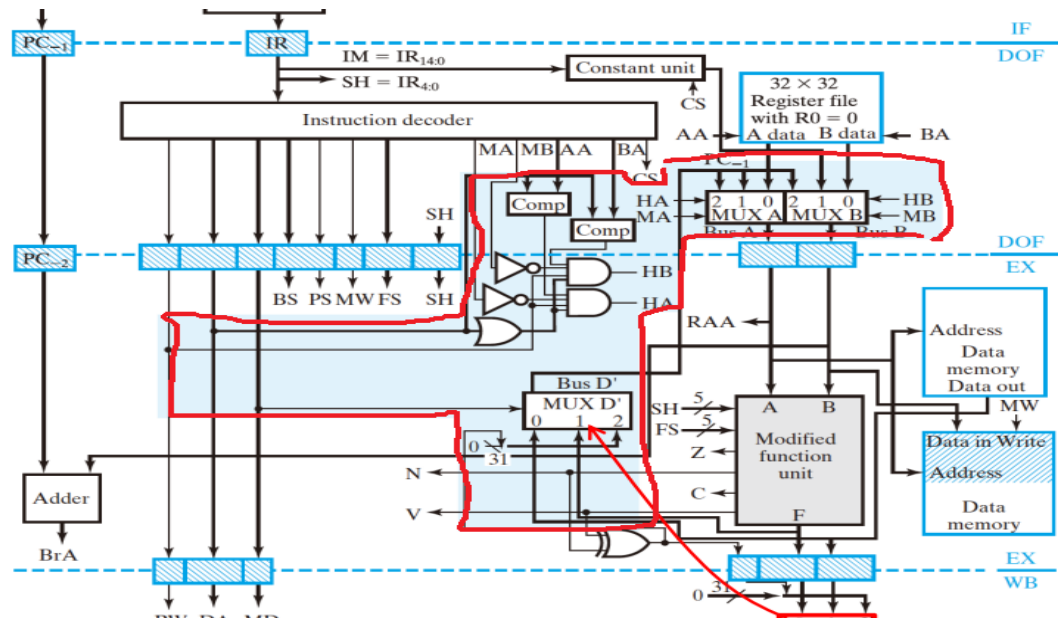在 **DOF_state** 時，有可能會發生 **data_hazard**，就是當 DOF 需要的 register 的值和要被 WB 回去的 register 或 EXE 中的 register 的值一樣的時候，因為還沒 write back，所以我解決的方法，就是使用 **Forwarding**，把現在 write_back 的值直接塞到 DOF 裡面，讓 DOF 可以取到正確的資訊，已完成這個 state。




```

always @(*) begin
if((EX_RW != 0) && (EX_DA != 5'b00000) && (MA == 0) && (EX_DA == DOF_AA))
begin
EX_Hazard_A = 1'b1;
end
else
begin
EX_Hazard_A = 1'b0;
end
if((EX_RW != 0) && (EX_DA != 5'b00000) && (MB == 0) && (EX_DA == DOF_BA))
begin
EX_Hazard_B = 1'b1;
end
else
begin
EX_Hazard_B = 1'b0;
end
if((WB_RW != 0) && (WB_DA != 5'b00000) && (MA == 0) && (WB_DA == DOF_AA))
begin
WB_Hazard_A = 1'b1;
end
else
begin
WB_Hazard_A = 1'b0;
end
if((WB_RW != 0) && (WB_DA != 5'b00000) && (MB == 0) && (WB_DA == DOF_BA))
begin
WB_Hazard_B = 1'b1;
end
else
begin
WB_Hazard_B = 1'b0;
end
end



```

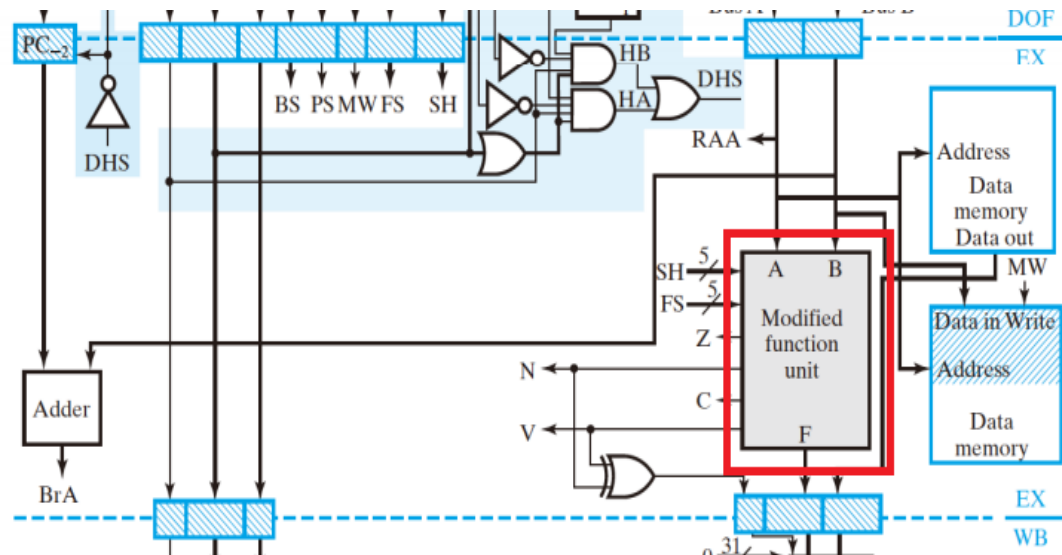下一個 state 就是 **EXE_state**，需要做 function_unit 的運算，此部分跟上次作業並無太大差別，最主要改變只有在 bit 數從 16bit 變成 32bit，而出來的值會需要和 D_memory 出來的值以及 N 和 Z 做 exclusive 的值進到 MUX_D，讓 **WB_state** 去做判斷看要取出哪一個值。



```
Function_Unit Function_unit(
.clk(clk),
.rst_n(rst_n),
.A(EX_BUS_A),
.B(EX_BUS_B),
.FS(EX_FS),
.SH(EX_SH),
.Z(Z),
.N(N),
.C(C),
.V(V),
.F(F)
);
```

  最後 **WB_state**，則是把值寫到 **register** 裡面，用 **MUX_D** 選出來的值，而此時 **PC** 會+1，而這時又會出現問題，因為如果出現 **branch** 的話，**PC** 值則會跳動，而這時前面讀進來的 **instruction** 則不能夠用，所以我就把讀進來的 **instruction** 給 **flush** 掉，而 **branch** 後的 **PC** 值，則是 **BRA** 和 **RAA** 這兩個 **register** 的值決定。



```

always @(*) begin //判断branch
    if(!DOF_flush) begin
        C_sel = {EX_BS[1], (((EX_PS ^ Z) | EX_BS[1])&EX_BS[0])};
    end else begin
        C_sel = 0;
    end
end

* MUXC */
always @(*) begin
    pc_next = pc + 1;
    case(C_sel)
        2'b01 : pc_next = BrA;
        2'b11 : pc_next = BrA;
        2'b10 : pc_next = RAA;
    endcase
end


endmodule

```

下面是我測試的 testcase :GCD 以及 Summation

 
1. GCD(27 和 12 的 GCD)

```
[          1290] Read Pipeline.I_mem.read_mem[00c]: 45200402
[          1310] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
[          1310] Read Pipeline.I_mem.read_mem[00d]: 40090800
[          1330] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
[          1330] Read Pipeline.I_mem.read_mem[00e]: 00000000
[          1350] Read Pipeline.d_mem.read_mem[402]: 00000000
[          1350] Read Pipeline.I_mem.read_mem[00f]: 00000000
[ *****Register[18] IS          3 *****
[          1370] Write to 00000003 Pipeline.d_mem.write_mem[402]
[          1370] Read Pipeline.I_mem.read_mem[010]: 00000000
[          1390] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
[          1390] Read Pipeline.I_mem.read_mem[011]: 00000000
[          1410] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
[          1410] Read Pipeline.I_mem.read_mem[012]: 00000000
[          1430] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
[          1430] Read Pipeline.I_mem.read_mem[013]: 00000000
[          1450] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
[          1450] Read Pipeline.I_mem.read_mem[014]: 00000000
[          1470] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
[          1470] Read Pipeline.I_mem.read_mem[015]: 00000000
[          1490] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
```




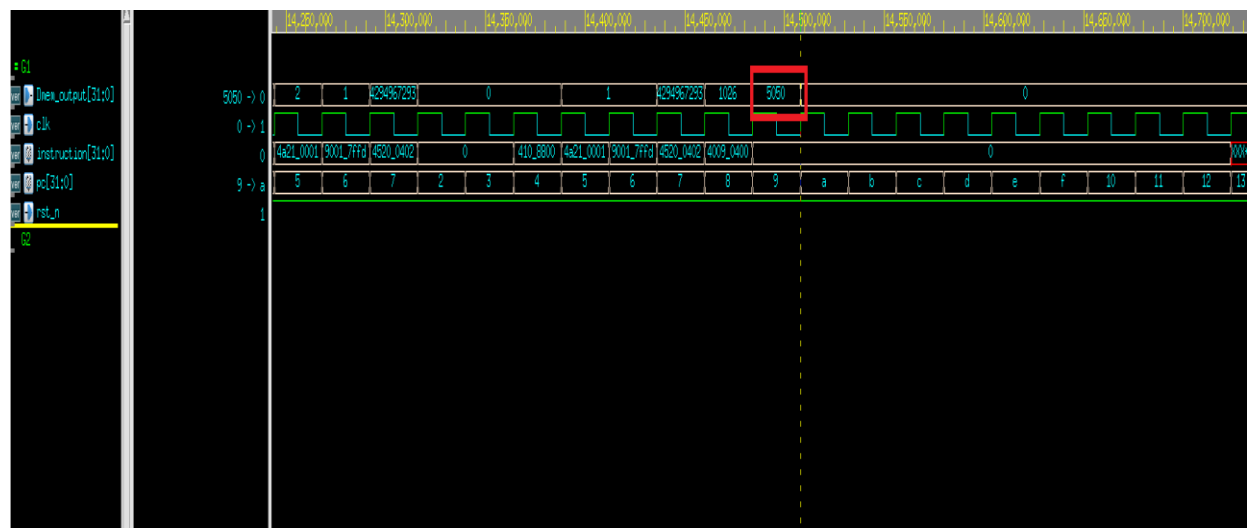2. Summation(1+~100)

```
[
    11970] Read Pipeline.I_mem.read_mem[003]: 4a210001
[
    11990] Read Pipeline.d_mem.read_mem[3b9]: xxxxxxxx
[
    11990] Read Pipeline.I_mem.read_mem[004]: 90017ffd
[
    12010] Read Pipeline.d_mem.read_mem[001]: xxxxxxxx
[
    12010] Read Pipeline.I_mem.read_mem[005]: 45200402
****Register[ 1] IS      5050 ****
[
    12030] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
[
    12030] Read Pipeline.I_mem.read_mem[006]: 40090400
****Register[ 2] IS      5050 ****
[
    12050] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
[
    12050] Read Pipeline.I_mem.read_mem[007]: 00000000
[
    12070] Read Pipeline.d_mem.read_mem[402]: xxxxxxxx
[
    12070] Read Pipeline.I_mem.read_mem[008]: 00000000
****Register[18] IS      5050 ****
[
    12090] Write to 000013ba Pipeline.d_mem.write_mem[402]
[
    12090] Read Pipeline.I_mem.read_mem[009]: 00000000
[
    12110] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
```



3. multiplication

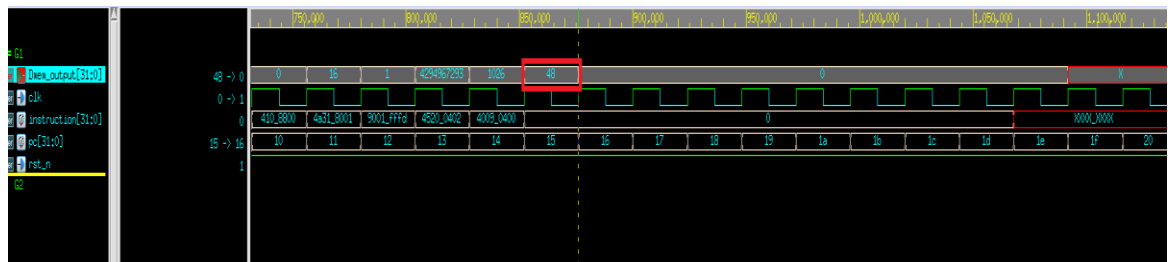

```

****Register[1] IS      48 ****
****Register[2] IS      16 ****
[      876] write to 00000030 Pipeline.d_mem.write_mem[402]
[      876] Read Pipeline.I_mem.read_mem[015]: 00000000
[      900] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
[      900] Read Pipeline.I_mem.read_mem[016]: 00000000


```

4. my_test

```

7260] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx
7260] Read Pipeline.I_mem.read_mem[007]: 00000000
7284] Read Pipeline.d_mem.read_mem[402]: xxxxxxxx
7284] Read Pipeline.I_mem.read_mem[008]: 00000000
****Register[1] IS      1275 ****
****Register[2] IS       0 ****
7308] Write to 000004fb Pipeline.d_mem.write_mem[402]
7308] Read Pipeline.I_mem.read_mem[009]: 00000000
7332] Read Pipeline.d_mem.read_mem[000]: xxxxxxxx

```

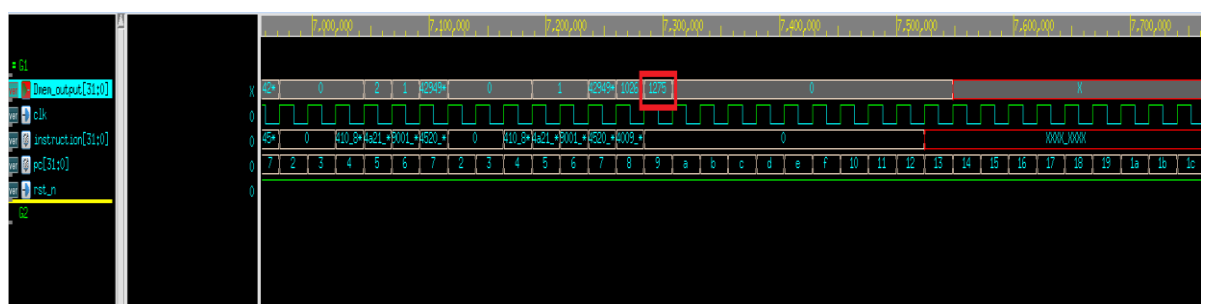

這次 project 遇到的困難其實蠻多的，一開始的讀檔進來就想了很久，最後研究出用 preload 這個參數弄進來，後面又發現，register 值會晚一個 cycle 近來，所以我就讓他早一個 cycle 先 preload 進來做判斷，還有 forwardind，因為一開始沒有使用 forwarding，所以跑出來的結果非常奇怪，最後才發現是因為 data_hazard 的關係。

Systhesis:

Timing Report:

| | | | |
|---------------------------------|-------|-------|---|
| Dmem_output_reg[21]/CK (EDFFXL) | 0.00 | 10.00 | r |
| library setup time | -0.33 | 9.67 | |
| data required time | | 9.67 | |
| ----- | | | |
| data required time | | 9.67 | |
| data arrival time | | -9.67 | |
| ----- | | | |
| slack (MET) | | 0.00 | |
| | | | |
| Startpoint: Dmem_input[6] | | | |
| (input port) | | | |
| Endpoint: Data_addr[6] | | | |
| (output port) | | | |
| Path Group: default | | | |
| Path Type: max | | | |
| Point | Incr | Path | |
| ----- | | | |
| input external delay | 0.00 | 0.00 | f |
| Dmem_input[6] (in) | 0.00 | 0.00 | f |
| U426/Y (A022X1) | 0.30 | 0.30 | f |
| Mux_A/Forward[6] (MUX_A) | 0.00 | 0.30 | f |
| Mux_A/U14/Y (A0I22XL) | 0.14 | 0.44 | r |
| Mux_A/U13/Y (NAND2XL) | 0.09 | 0.53 | f |
| Mux_A/Bus_A[6] (MUX_A) | 0.00 | 0.53 | f |
| U331/Y (0AI2BB2XL) | 0.17 | 0.70 | f |
| Data_addr[6] (out) | 0.00 | 0.70 | f |
| data arrival time | | 0.70 | |
| | | | |
| max_delay | 10.00 | 10.00 | |
| output external delay | 0.00 | 10.00 | |
| data required time | | 10.00 | |
| ----- | | | |
| data required time | | 10.00 | |
| data arrival time | | -0.70 | |
| ----- | | | |
| slack (MET) | | 9.30 | |

Area report:

Report : area
Design : pipeline
Version: K-2015.06-SP1
Date : Wed Jan 18 01:17:40 2017

Library(s) Used:

slow (File: /theda21_2/CBDK_IC_Contest/cur/SynopsysDC/db/slow.db)


Number of ports: 1403
Number of nets: 7228
Number of cells: 5842
Number of combinational cells: 4434
Number of sequential cells: 1397
Number of macros/black boxes: 0
Number of buf/inv: 865
Number of references: 52

Combinational area: 46019.907791
Buf/Inv area: 4812.128930
Noncombinational area: 43894.762604
Macro/Black Box area: 0.000000
Net Interconnect area: undefined (No wire load specified)


Total cell area: 89914.670395
Total area: undefined

***** End Of Report *****

合成後的 gcd:

 

合成過後的 summation:

 

Timing diagram showing the execution of the 'addi' instruction. The diagram includes signals: den_output[31:0], clk, instruction[31:0], pc[31:0], and rst_n. The 'den_output' signal is highlighted with a red box, showing a value of 1. The 'instruction' signal shows the binary value 00000001000000000000000000000000. The 'pc' signal shows the binary value 00000000000000000000000000000000. The 'rst_n' signal is high. The 'clk' signal is a periodic clock. The 'den_output' signal is high for one clock cycle, indicating the completion of the instruction.

一開始的問題是，當 RAM 還沒有 output 出來時，我的 instruction_next，就會先讀到值，所以會是 unknow，導致後面都讀不到值，而後面則是合成過後的 delay，會導致我讀值全部慢一個 cycle，後來我讓 clk 也 delay，就解決了這個問題。

完成部分;

Completion

1. Four-stage pipeline (完成)
2. Data forwarding for data hazard (完成)
3. Branch prediction (完成)
4. My testcase design (完成)
5. Synthesis (完成)

心得:

這次的 final project，讓我真正的了解到合成的奧妙所在，也是做得最久的一次，也讓我好好的去研究合成這個東西，及它會造成的效果，而最後看到結果也非常開心。

也謝謝助教和教授幫伍們 debug，最後祝助教和教授春節快樂。